

NM6007 Lab 1: Analog IC Design

Design of a Wide-band Amplifier from schematic to layout verification.